

Problem 6.5

The current in a 20 mH inductor is known to be

$$i(t) = \begin{cases} 40 \text{ mA} & t \leq 0 \\ A_1 e^{-10000t} + A_2 e^{-40000t} & t \geq 0 \end{cases}$$

i) Choose the correct expression for the voltage across the inductor for $t > 0$:

$$v(t) = L \frac{di}{dt}$$

$$v(t) = (20 * 10^{-3}) * \frac{d}{dt}(A_1 e^{-10000t} + A_2 e^{-40000t})$$

$$v(t) = (20 * 10^{-3}) * (-10000A_1 e^{-10000t} - 40000A_2 e^{-40000t})$$

$$v(t) = 200A_1 e^{-10000t} - 800A_2 e^{-40000t}$$

This is the voltage across the inductor at time $t > 0$. The initial voltage in the inductor is, $v(0) = 28 \text{ V}$. Since $v(t) = 200A_1 e^{-10000t} - 800A_2 e^{-40000t}$, $v(0) = 200A_1 - 800A_2$.

$$28 = 200A_1 - 800A_2 \quad (1)$$

The equation for the current can then be used, $i(t) = A_1 e^{-10000t} + A_2 e^{-40000t}$, where $i(0) = A_1 + A_2$

$$40 * 10^{-3} = A_1 + A_2 \quad (2)$$

Solving these two equations:

$$A_1 = 0.1$$

$$A_2 = -0.06$$

Now to get the final answer for the voltage as a function of time, the values of A_1 and A_2 are substituted:

$$v(t) = -20e^{-10000t} + 48e^{-40000t}$$

ii) Find the time, greater than zero, when the power at the terminals of the inductor is zero.

$$power = iv = iL \frac{di}{dt}$$

$$power = (0.1e^{-10000t} - 0.06e^{-40000t})(-20e^{-10000t} + 48e^{-40000t})$$

$$power = -2e^{-20000t} + 4.8e^{-50000t} + 1.2e^{-50000t} - 2.88e^{-80000t}$$

$$power = -2e^{-20000t} + 6e^{-50000t} - 2.88e^{-80000t}$$

$$0 = -2e^{-20000t} + 6e^{-50000t} - 2.88e^{-80000t}$$

Setting $e^{-20000t} = x$,

$$0 = -2x + 6x^{2.5} + 2.88x^4$$

$$x = 0 \quad x = \left(\frac{5}{12}\right)^{\frac{1}{1.5}}$$

$$e^{-20000t} = \left(\frac{5}{12}\right)^{\frac{1}{1.5}}$$

$$t = 29.18 \mu s$$

Problem 6.12

Initially there was no energy stored in the 5 H inductor in the circuit in the following figure when it was placed across the terminals of the voltmeter. At $t = 0$ the inductor was switched instantaneously to position b where it remained for 1.6 s before returning instantaneously to position a. The d'Arsonval voltmeter has a full-scale reading of 28 V and a sensitivity of 1000 Ω/V .

i) What will the reading of the voltmeter be at the instant the switch returns to position a if the inertia of the d'Arsonval movement is negligible?

$$i(t) = \frac{1}{L} \int_0^t v(t) dt$$

$$i(t) = \frac{1}{5} \int_0^t (3 * 10^{-3}) dt$$

$$i(t) = \frac{3 * 10^{-3}}{5} t$$

$$i(1.6) = \frac{3 * 10^{-3}}{5} (1.6) = 0.00096 \text{ A}$$

The full scale reading of the meter is 28 V, and the sensitivity is 1000 Ω/V , therefore, the resistance of the meter is $28 * 1000 \frac{V}{\Omega} = 28000 \Omega$.

$$V = iR$$

$$V = (0.00096)(28000) = \boxed{26.88 \text{ V}}$$

Problem 6.14

The voltage at the terminals of the capacitor in is known to be:

$$v(t) = \begin{cases} -10 \text{ V} & t \leq 0 \\ 40 - 1e^{-1000t}(50 \cos(500t) + 20 \sin(500t)) \text{ V} & t \geq 0 \end{cases}$$

where t is in seconds. Assume $C = 0.8 \mu F$.

i) Find the current in the capacitor for $t > 0$.

$$i(t) = C \frac{dv}{dt}$$

$$i(t) = (0.8) \frac{d}{dt} (40 - 1e^{-1000t}(50 \cos(500t) + 20 \sin(500t)))$$

$$i(t) = 0.8e^{-1000t} (45000 \sin(500t) + 40000 \cos(500t))$$

$$i(t) = e^{-1000t} (36000 \sin(500t) + 32000 \cos(500t)) \text{ A}$$

$$\boxed{i(t) = e^{-1000t} (36 \sin(500t) + 32 \cos(500t)) \text{ mA}}$$

ii) How much energy (in millijoules) is stored in the capacitor at $t = \infty$?


$$v(t) = 40, t = \infty$$

$$w = \frac{1}{2} C v^2$$

$$w = \frac{1}{2} (0.8) (40)^2$$

$$w = 0.64 \text{ mJ}$$

Problem 6.34

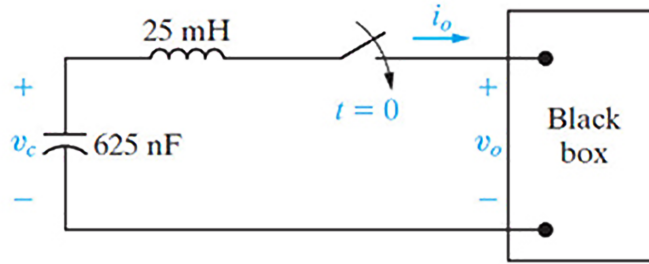

At $t = 0$ a series-connected capacitor and inductor are placed across the terminals of a black box, as shown in Figure 1. For $t > 0$:

$$i_0 = 1.5e^{-16000t} - 0.5e^{-4000t} \text{ A}$$

Voltage across the capacitor: $v(0) = -50 \text{ V}$

$$v(t) = -\frac{1}{C} \int_0^t i_0 dt + v(0)$$

$$v(t) = -\frac{1}{625 * 10^{-9}} \int_0^t (1.5e^{-16000t} - 0.5e^{-4000t}) dt - 50$$

$$v(t) = -\frac{1}{625 * 10^{-9}} * \frac{1}{32000} (e^{-16000t} (4e^{12000t} - 3) - 1) - 50$$

$$v(t) = -50(e^{-16000t} (4e^{12000t} - 3) - 1) - 50$$

$$v(t) = -50e^{-16000t} (4e^{12000t} - 3)$$

$$v(t) = 150e^{-16000t} - 200e^{-4000t} \text{ V}$$

Voltage across the inductor:

$$v(t) = L \frac{di}{dt}$$

$$v(t) = 25 * 10^{-3} \frac{d}{dt}(1.5e^{-16000t} - 0.5e^{-4000t})$$

$$v(t) = e^{-16000t}(50e^{12000t} - 600)$$

v_0 will equal $v_c - v_l$:

$$v_0 = (150e^{-16000t} - 200e^{-4000t}) - (e^{-16000t}(50e^{12000t} - 600))$$

$$\boxed{v_0 = 750e^{-16000t} - 250e^{-4000t} \text{ V}}$$